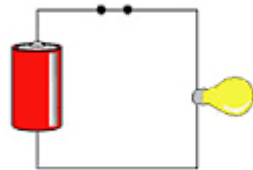



Closed Circuit

A circuit that has a complete path for current to flow




Open Circuit

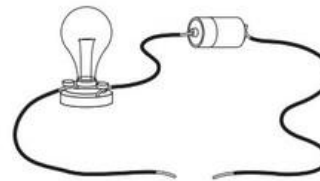A broken path so current cannot flow, which means that it is not functional



Parallel circuit

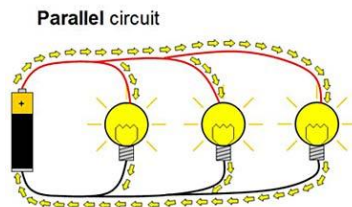A circuit in which the loads are arranged with multiple paths to take



Series Circuit

A circuit in which loads are arranged in a chain, so that the current has only one path to take.

